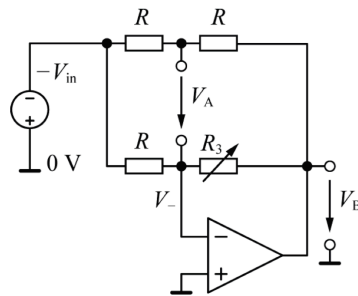



The circuit shown is a Wheatstone bridge that measures an unknown variable electrical resistance by balancing its two branches – one with the unknown component.

1. Find the expressions for the Thevenin voltage  $V_{th}$  [1p] and Thevenin resistance  $R_{th}$  [1p] of the circuit so that variable resistor  $R_3$  appear in the numerator. The two terminals for this problem are the points where bridge voltage  $V_A$  is measured. Express  $V_A$  in terms of  $V_{th}$ ,  $R_{th}$  and the measuring resistance  $R_m$  that would be present across the terminals if a voltmeter were connected. [0.5p]
2. The bridge is balanced when  $R_1 = R_2 = R_3 = R_4 = R$ . Simplify the expression for the bridge voltage as a function of the variable resistor  $R_3 = R + \Delta r$  and the measuring resistance  $R_m$ , that is  $V_A(\Delta r; R; R_m)$ . [1p] If  $V_{in} = 5\text{ V}$ ,  $R = 2\text{ k}\Omega$  and  $R_m = 100\text{ k}\Omega$ , calculate the  $V_A$  values for  $\Delta r = \{-1\text{ k}\Omega; 0\text{ k}\Omega; +1\text{ k}\Omega\}$ . [1p]



Now, we remove voltage source  $+V_{in}$  from the circuit and drive the bridge with an ideal op-amp as shown.

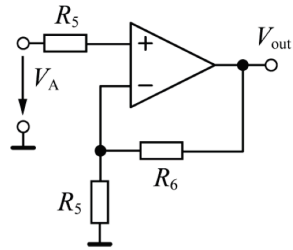3. What is the potential  $V_-$  of the inverting node and why? [0.5p] Express the op-amp voltage  $V_B$  in terms of  $R$ ,  $R_3$  and  $V_{in}$  when nothing is connected to read  $V_A$  and explain why this expression is simple! [1p] Express the bridge voltage as a function of the variable resistor  $R_3 = R + \Delta r$  and  $V_{in}$ , that is  $V_A(\Delta r; R; V_{in})$ . [1p]
4. Calculate  $V_A(\Delta r)$  again for  $V_{in} = 5\text{ V}$ ,  $R = 2\text{ k}\Omega$  and  $\Delta r = \{-1\text{ k}\Omega; 0\text{ k}\Omega; +1\text{ k}\Omega\}$ . [0.5p] Comparing the values to those in Problem-2, what are the advantages of this circuit in terms of  $V_A(\Delta r)$  linearity and symmetry? [1p]



To take advantages of the circuit in Problem-3, reading of  $V_A$  is done with the circuit shown next.

5. What is the current that flows through  $R_5$  into the non-inverting input? **[0.5p]** Express the output voltage in terms of the bridge voltage that is  $V_{out}(V_A)$ ! **[1p]**