

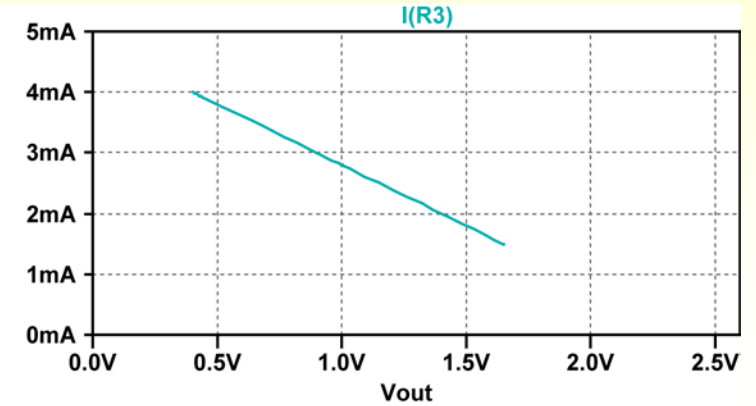


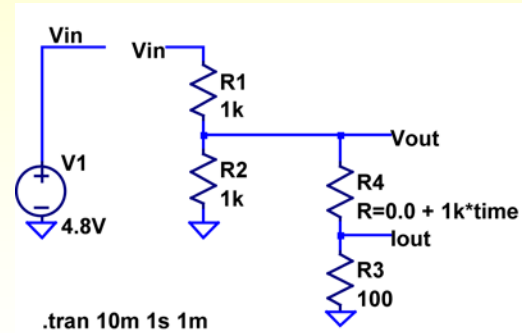

Resistive nets


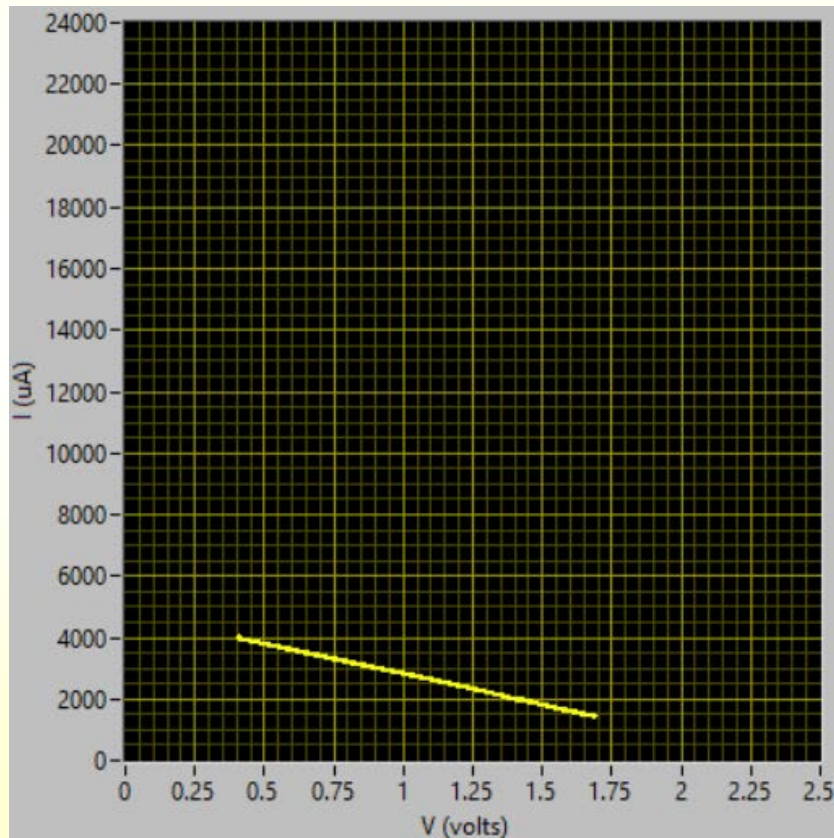
- Divider with resistive load
($V_{in} = +4.8V$)



Simulation

Op-amps

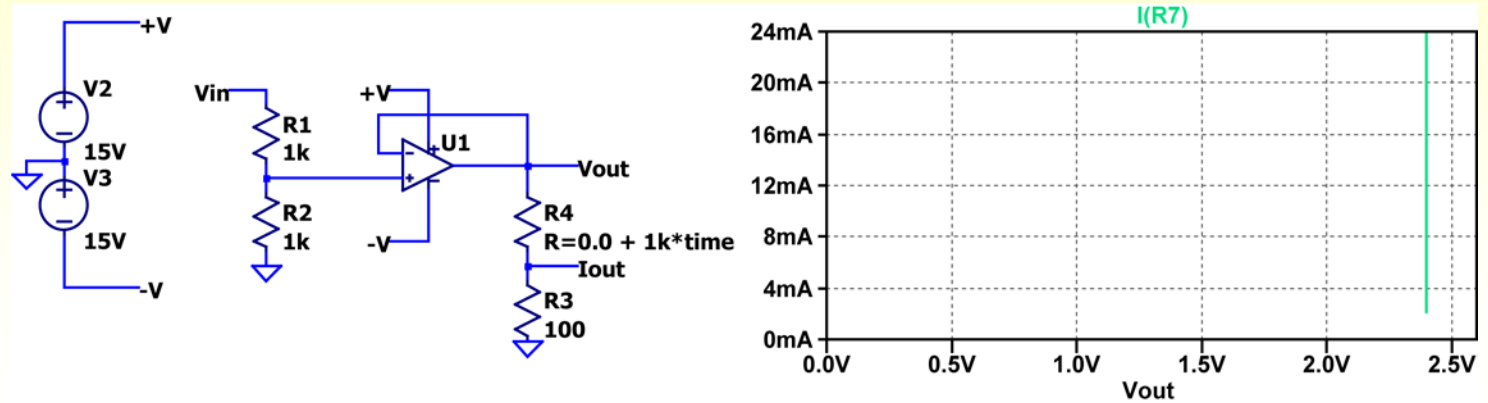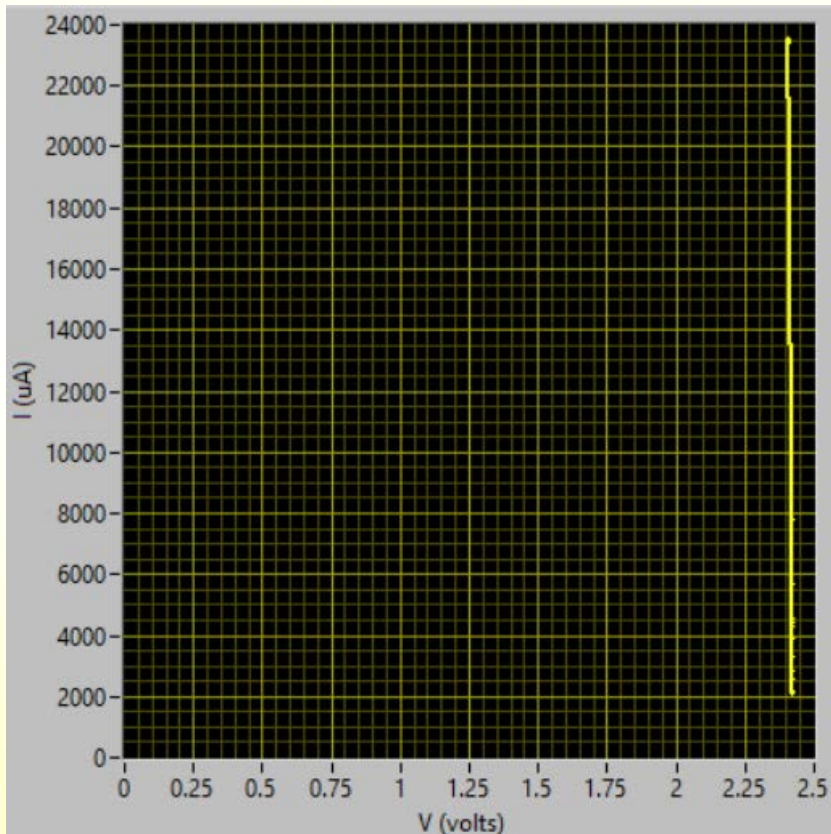- Divider with voltage follower ($V_{in} = +4.8V$)



Simulation

Op-amps

- Open-loop comparator: $V_{\text{comp}} = A_{\text{OL}}(V_{\text{in}}^+ - V_{\text{ref}}^-)$

